

LIGHTOR




Six - Channel Digitally - Controlled (Color) Light Organ

What's a Light Organ?

A Light Organ (or Color Organ) is a sound-to-light device which allows one to “see” sounds and music through a display of colored lights

Typical Light Organ Block Diagram

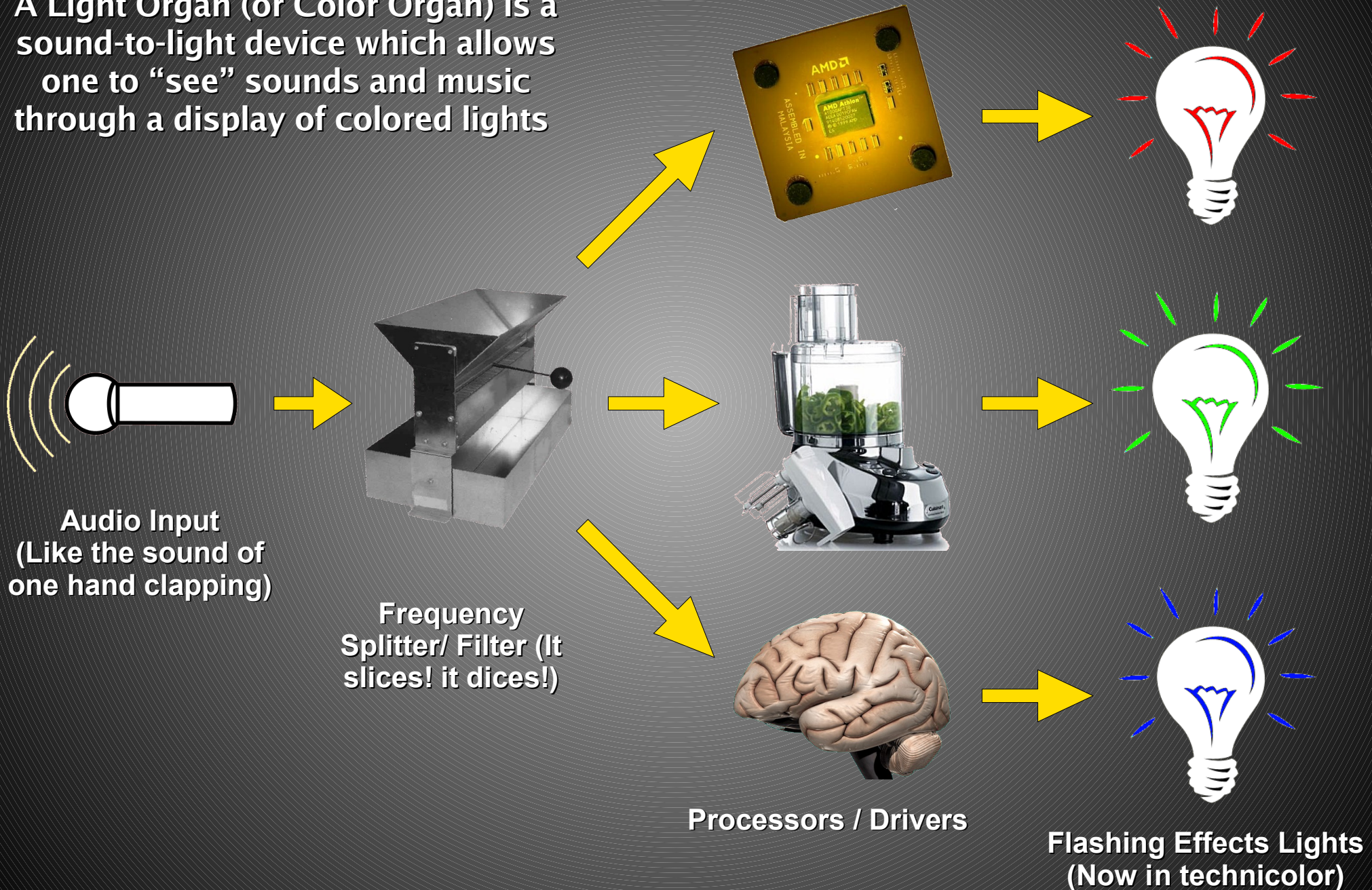

Design Comparison


Traditional Light Organs:

- Fully analog designs
- Usually use coarse RC filters
- Typically 3-channel designs for lows (100Hz), mids (1kHz), and highs (3kHz)
- Mediocre performance due to their often “low” tech implementations







The Lightor Design:

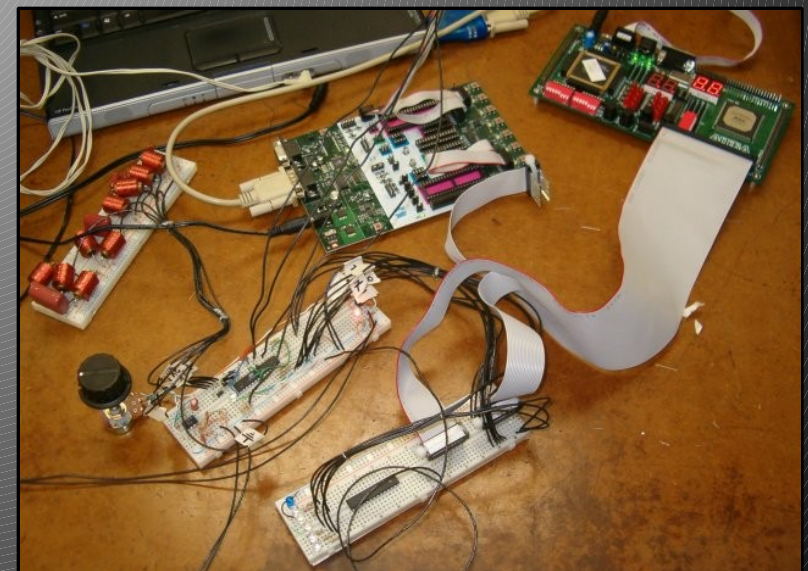- Analog/ digital hybrid design
- Resonant RLC filters for tighter control
- 6-channel (60Hz, 250Hz, 500Hz, 1kHz, 3kHz, 6kHz) design aims to provide more clarity across the audible spectrum and more flashing lights mean extra fun
- Dimming/ flashing of the lights is achieved using 8-bit PWM for precise control of the light show.











Preamp [Input] Stage

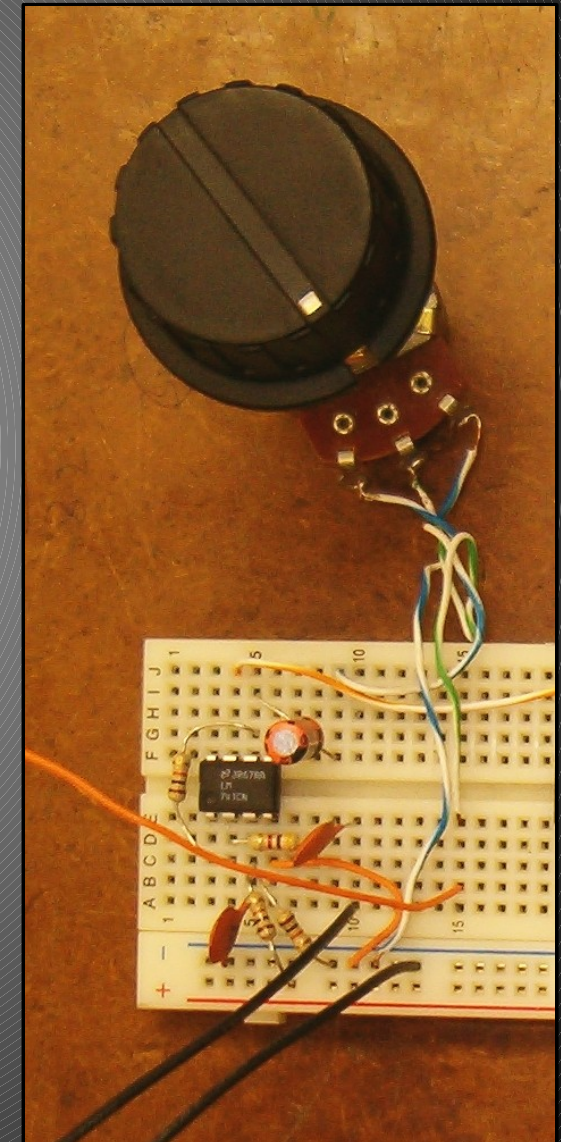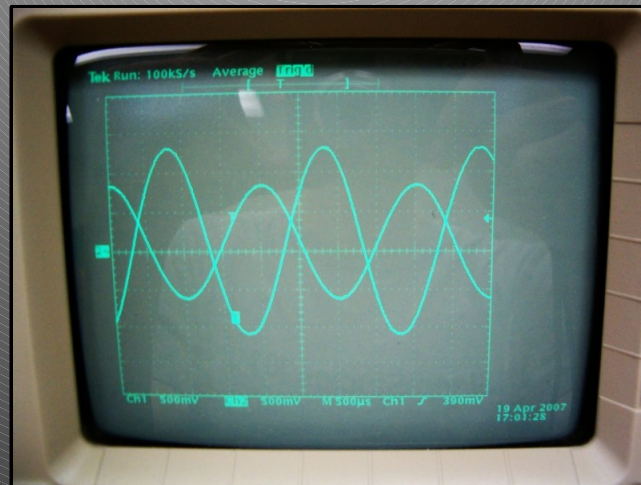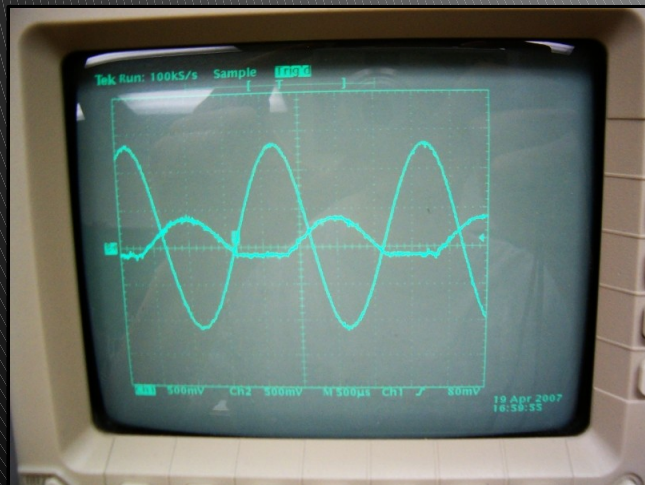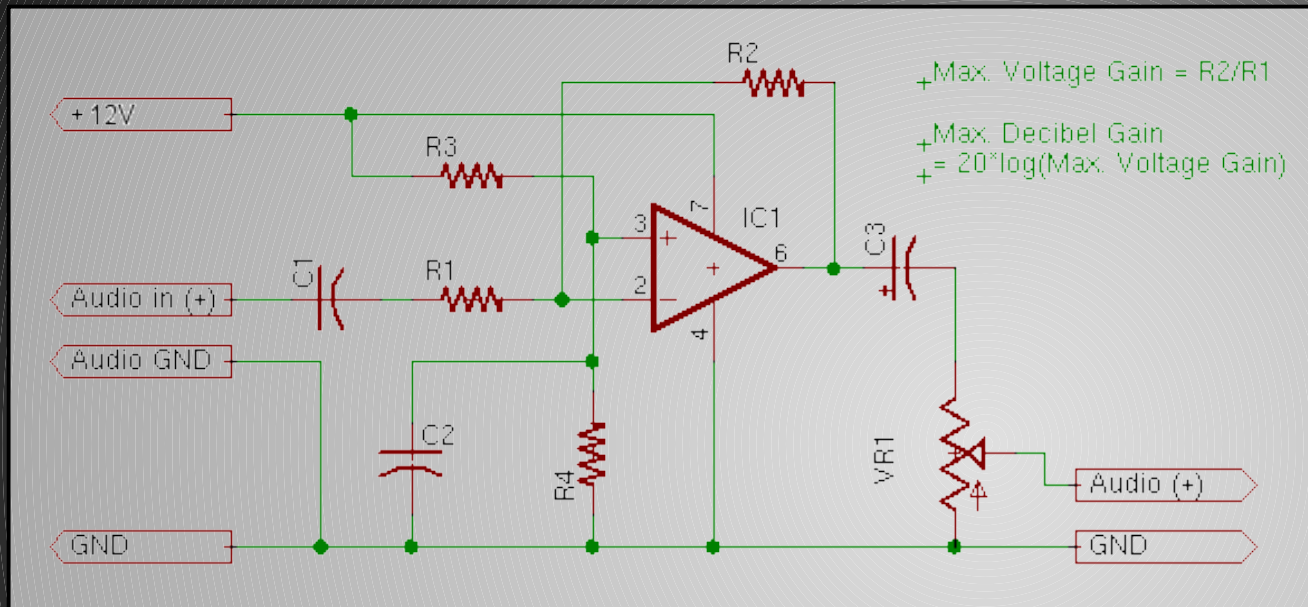The Preamp Stage uses a simple op-amp circuit to amplify the inputted line-level audio signal to a more usable level






Filter Stage

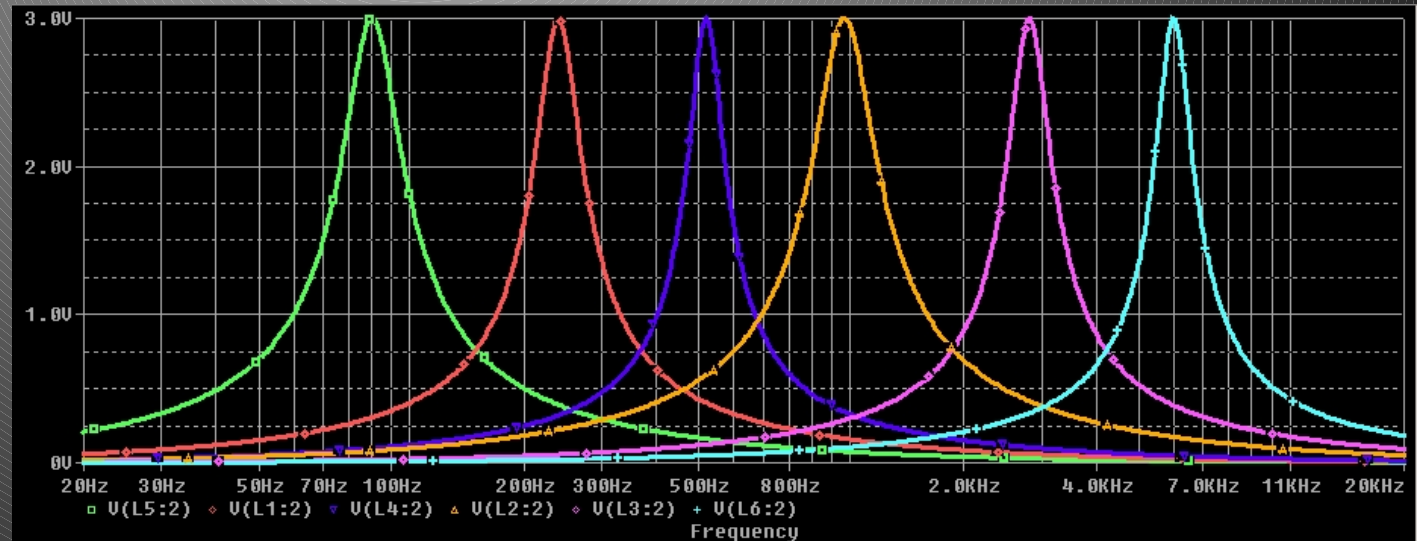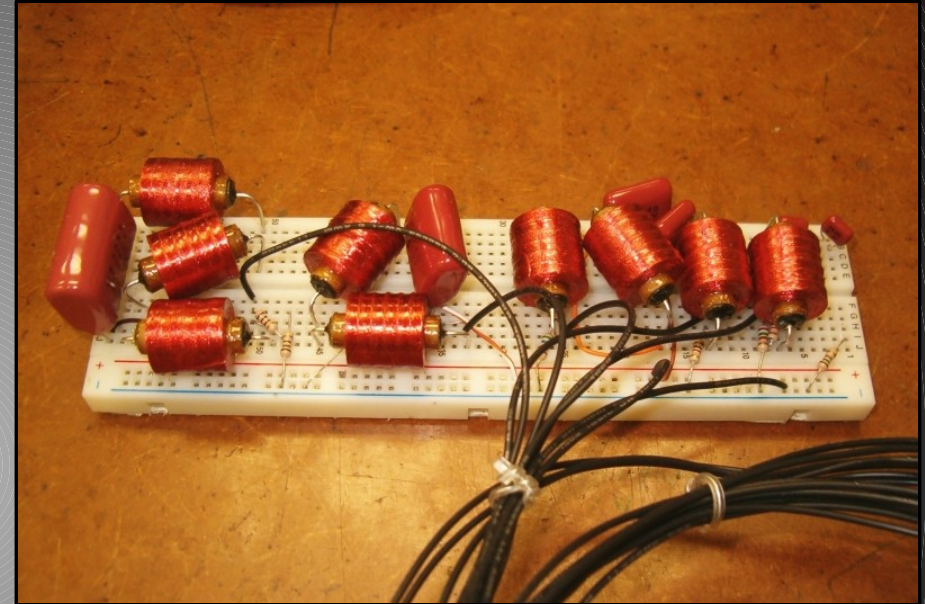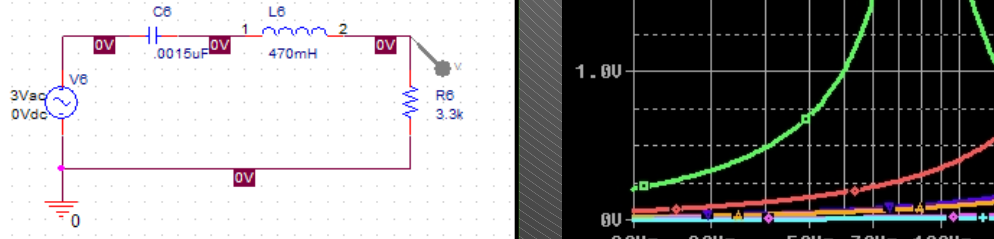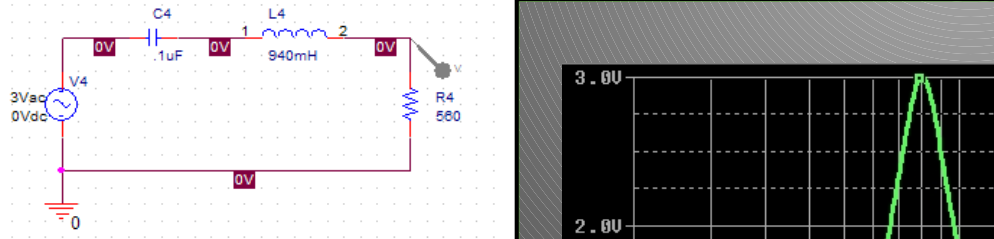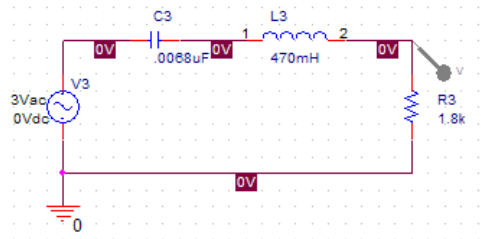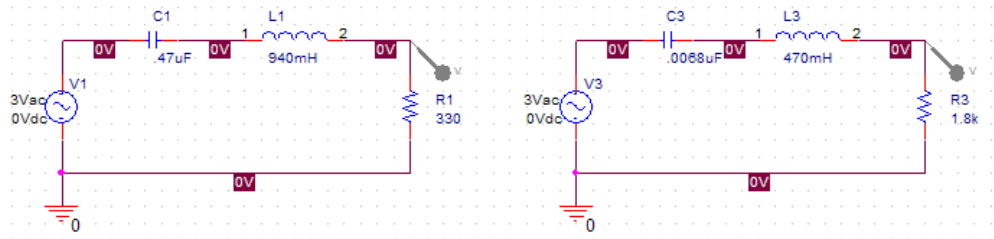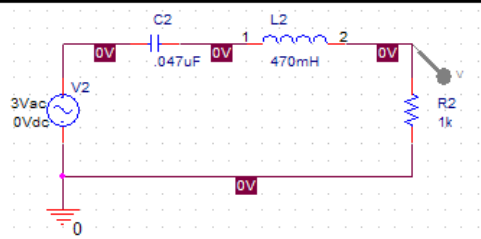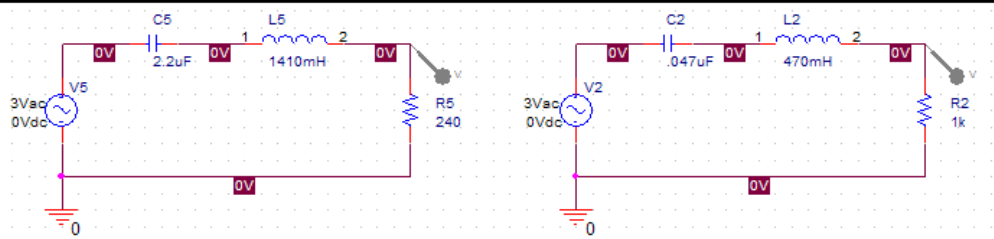The Filter Stage uses capacitors, resistors, and inductors to form six resonant band-pass filters tuned to six frequencies across the audible spectrum



Conversion Stage

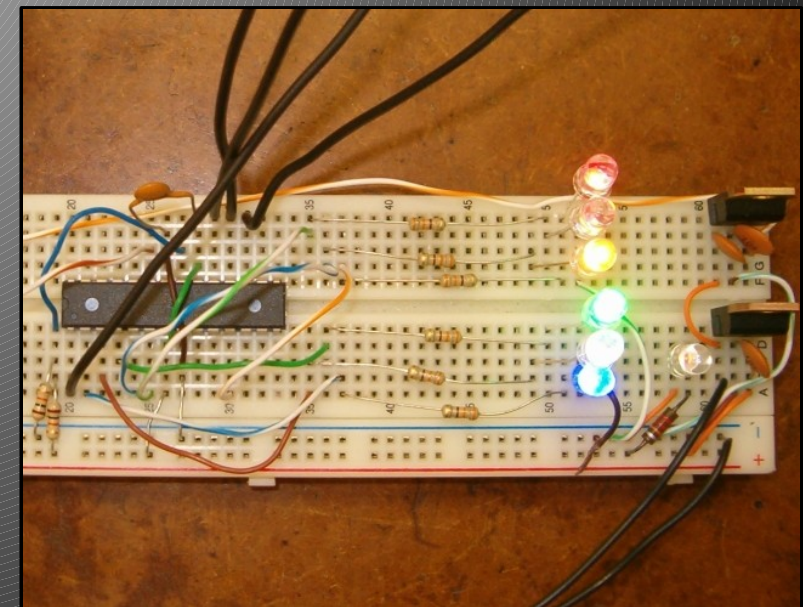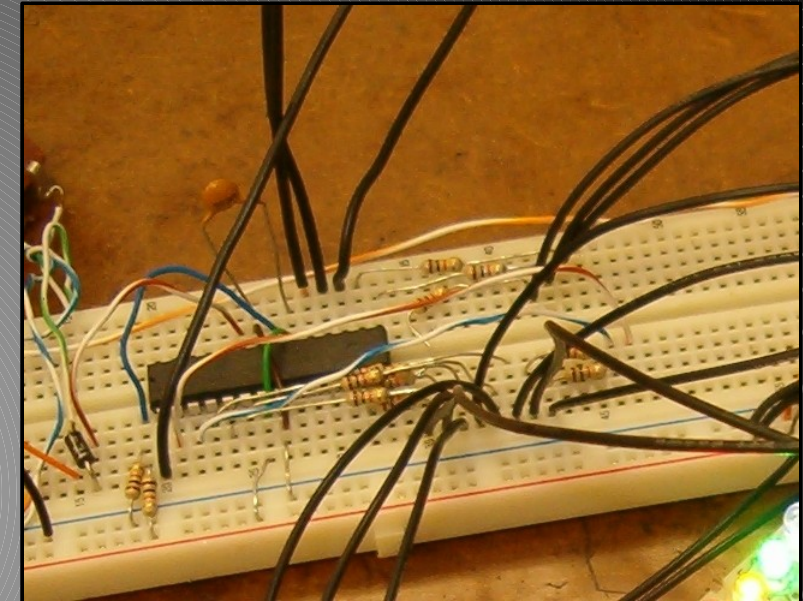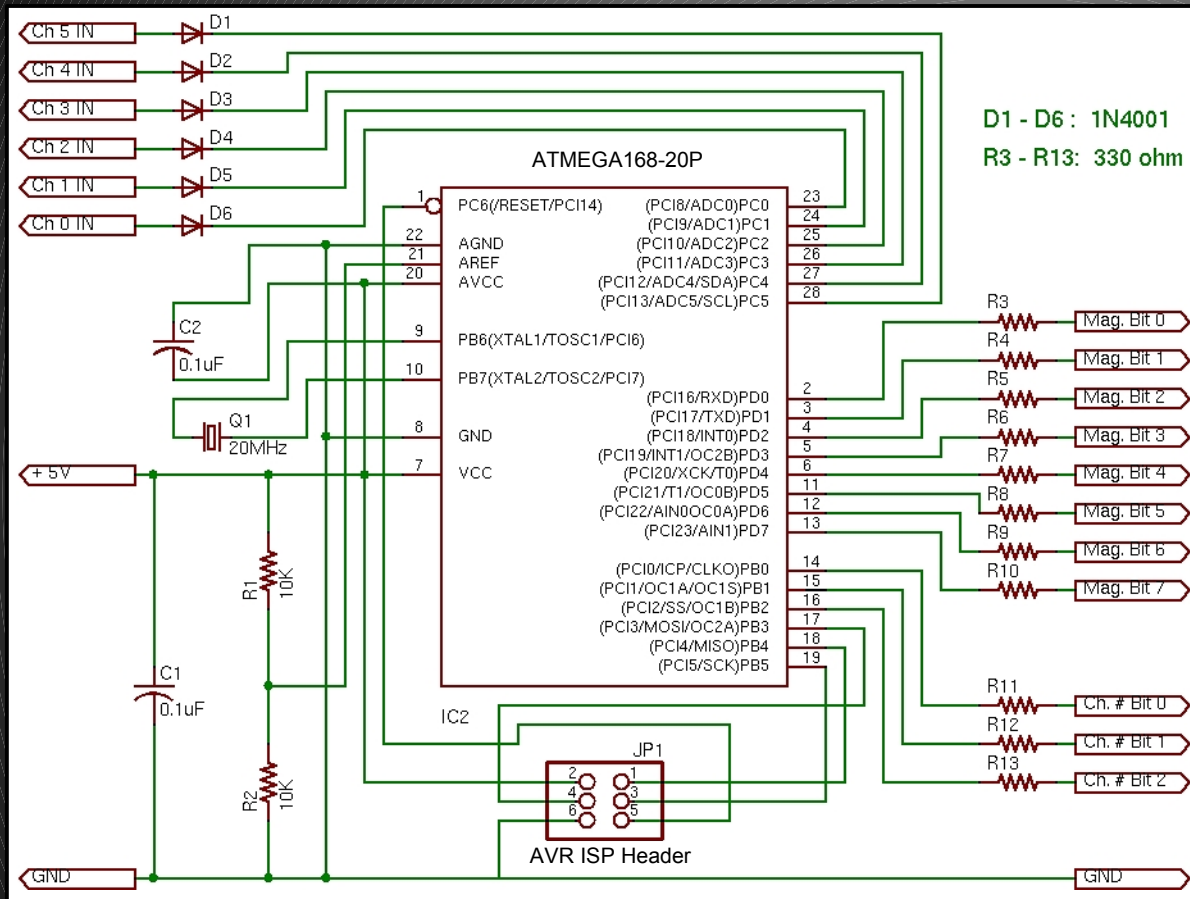The Conversion Stage uses a microcontroller with integrated ADC to convert the audio signals to 8-bit binary numbers which it then multiplexes and outputs





```

if (ADMUX == 0b00100000) {
    PORTB = 0b00000000; // Send the channel # out on PORTD
    PORTD = adc_res1; // Send the magnitude # out on PORTB
    ADMUX = 0b00100001; // Change to the next ADC channel
    ADCSRA |= _BV(ADSC); // Begin another ADC conversion (set "1")
}
else if (ADMUX == 0b00100001) {
    PORTB = 0b00000001; // Send the channel # out on PORTD
    PORTD = adc_res1; // Send the magnitude # out on PORTB
    ADMUX = 0b00100010; // Change to the next ADC channel
    ADCSRA |= _BV(ADSC); // Begin another ADC conversion (set "1")
}
    
```

Main [PWM] Stage

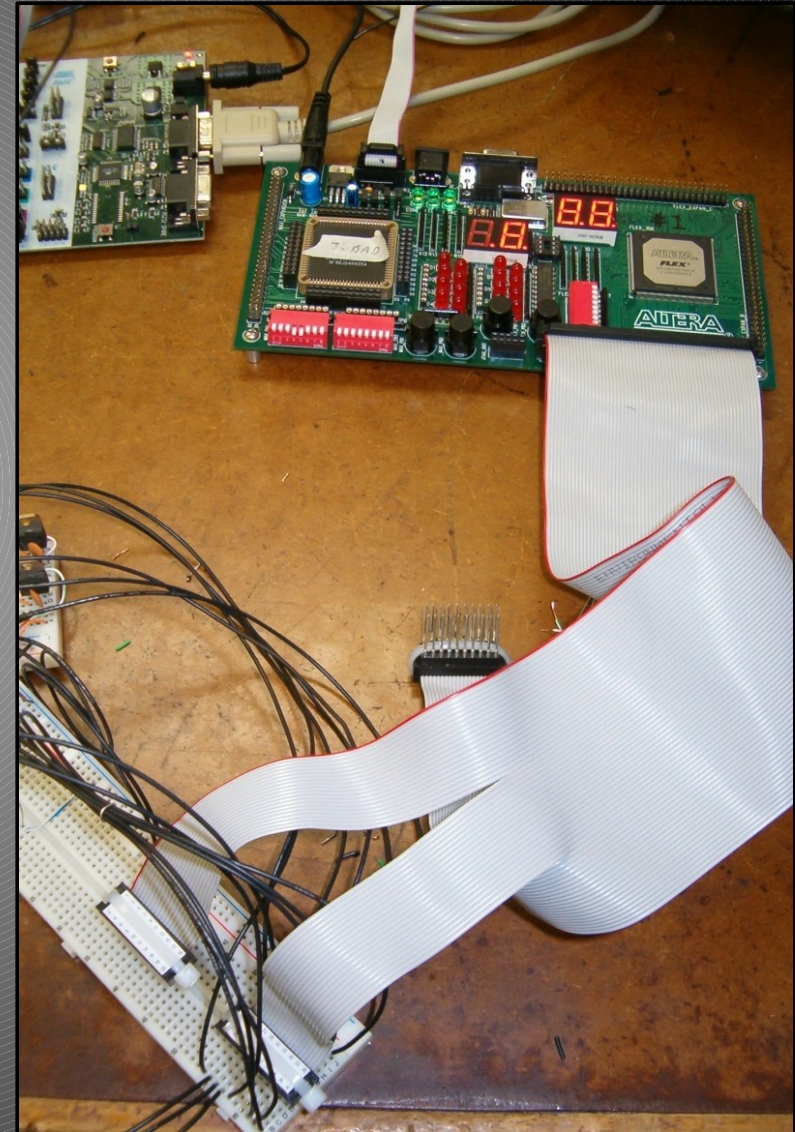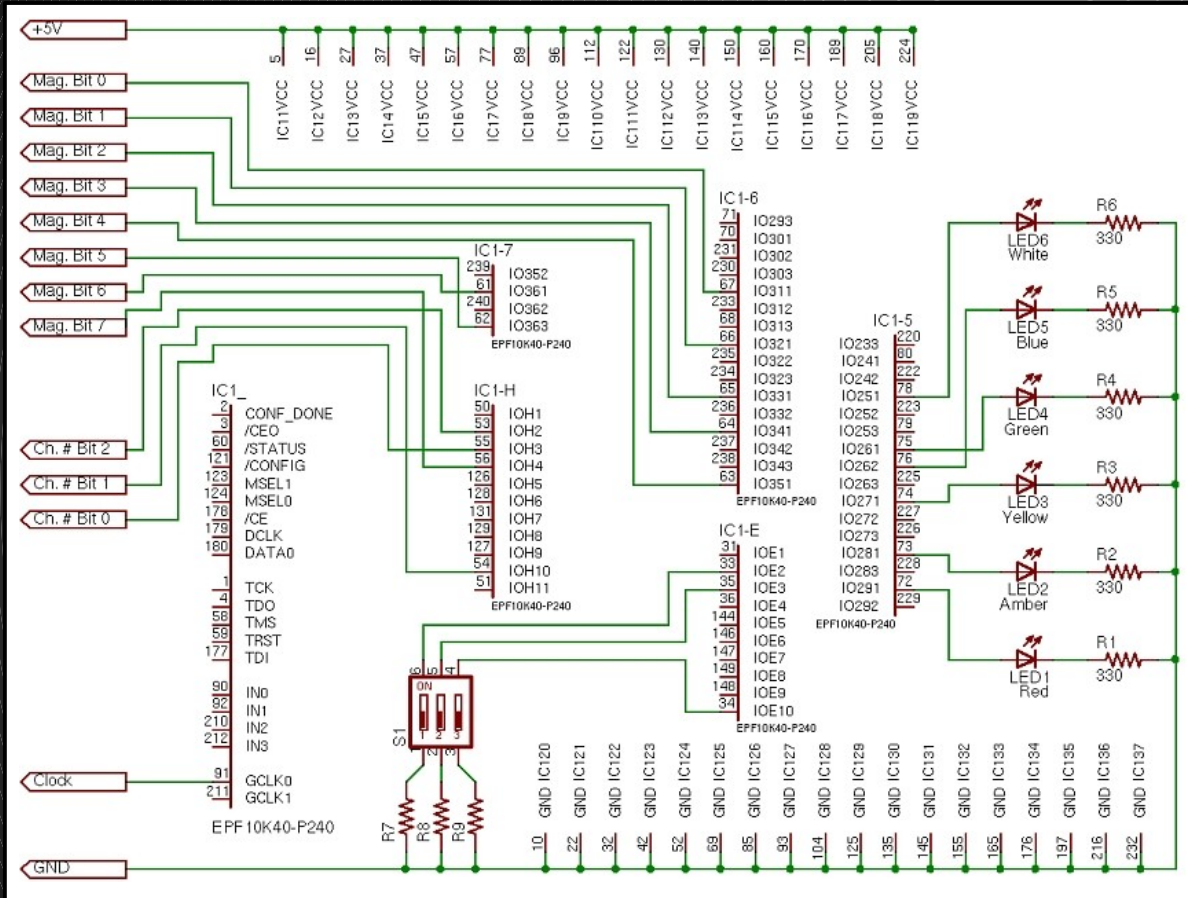The Main Stage collects & processes data from the Conversion Stage. It controls the voltage of each output channel based on that data using Pulse Width Modulation



```

pwm := pwm + '1';          -- Increment the main PWM counter
if (pwm > "11111111") then -- Check for counter overflow
    pwm := "00000000";    -- Start over again
end if;

if (pwm <= per0) then output0 <= '0'; -- Channel 0 PWM routine
else output0 <= '1';      -- Turn off the output
end if;                   -- Now light it up!

if (pwm <= per1) then output1 <= '0'; -- Channel 1 PWM routine
else output1 <= '1';      -- Turn off this output
end if;                   -- Now light it up!
    
```

Finishing It Off

To evolve Lightor from a prototype to a more polished, finished “product” consider:

- **Add a power stage** (to allow the driving of line-voltage, higher power loads)
- Use either **real audio-grade inductors** or switch to **RC filters** for tighter frequency control
- **Add averaging capabilities** to the main stages' VHDL code – to reduce jitteriness of the lights
- **More “fun” features**, such as the ability to rotate which outputs respond to which frequencies

